
### SWITCH MODE POWER SUPPLY (SMPS)

#### What is a Power Supply?

The power supply can be defined as it is an electrical device used to give electrical supply to electrical loads. The main function of this device is to change the electrical current from a source to the accurate voltage, frequency and current to supply the load. Sometimes, these power supplies can be named to as electric power converters.

#### **Power Supply Block Diagram**

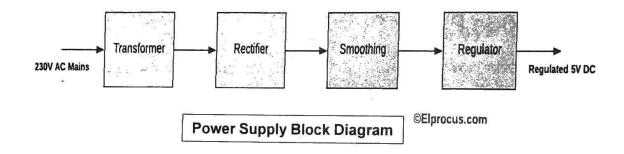


## Classification of Power Supply and Its Different Types

	OUTPUT = DC	OUTPUT = AC
INPUT = AC	Wall wart Bench power supplies Battery charger	Isolation transformer Variable AC supply Frequency changer
INPUT = DC	DC-DC converter	Inverter Generator UPS
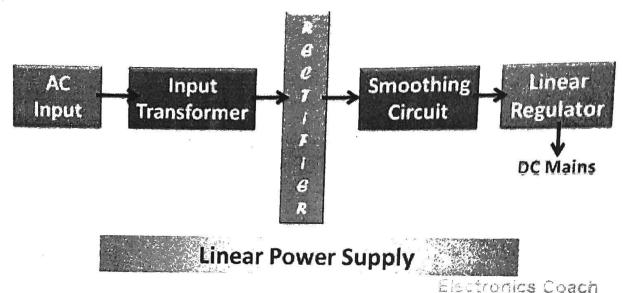
#### **Linear Power Supply**


The Linear Power Supply is power supplying circuit which is used in electrical and electronic circuit to supply the DC power to the circuit. It consists of a step-

down transformer, rectifier, a filter circuit and voltage regulator. It completes the stepping down of AC voltage first then it converts it into DC.


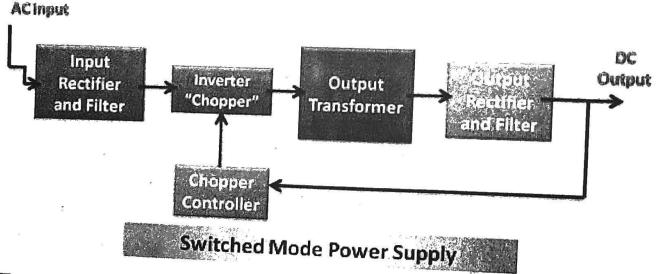
#### **Switched Mode Power Supply**

The Switched Mode Power Supply operated on the principle of switching using a MOSFET transistor. It consists rectifier circuit, a filter circuit, chopper, chopper controller, output transformer and a filter circuit. It converts the input signal into DC first then it steps down the voltage up to desired level.



#### Types of SMPS


Electronics Coach

- 1. D.C. to D.C. Converter:
- 2. Forward Converter:
- 3. Fly back Converter:
- Self-Oscillating Fly Back Converter:

# **Comparison Chart**

PARAMETERS	LINEAR POWER SUPPLY	SWITCH MODE POWER SUPPLY (SMPS)
Definition	It completes the stepping down of AC voltage first then it converts it into DC.	It converts the input signal into DC first then it steps down the voltage up to desired level.
Efficiency	Low efficiency i.e. about 20- 25%	High Efficiency i.e. about 60-65%
Voltage Regulation	Voltage regulation is done by voltage regulator.	Voltage regulation is done by feedback circuit.
Weight	It is bulky.	It is less bulky in comparison to linear power supply.
Reliability	More reliable in comparison to SMPS.	its reliability depends on the transistors used for switching
Complexity	Less complex than SMPS.	More complex than Linear power supply.
Transient response	It possess faster response.	It possess slower response.
RF interference	No RF interference	RF shielding is required as switching produces more RF interference.
Noise and Electromagnetic interference	It is immune to noise and electromagnetic interference.	Effect of noise and electromagnetic interference is quite significant, thus EMI filters are required.
Applications	Used in Audio frequency applications and RF applications.	Used in chargers of mobile phones, DC motors etc.
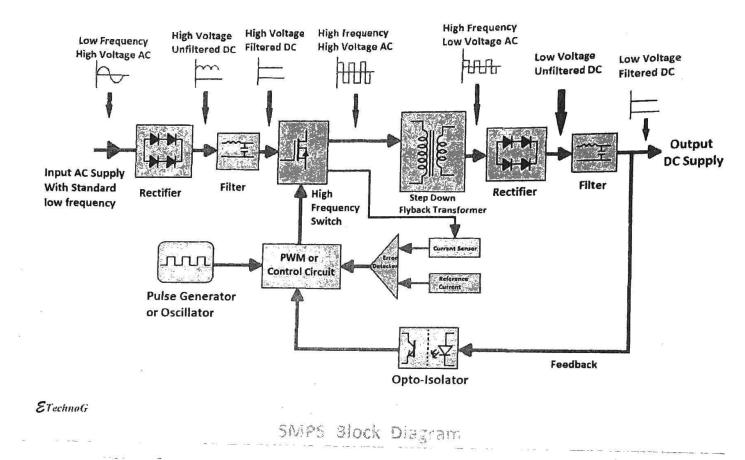
#### Block Diagram of SMPS for AC to DC converter



# Switched Mode Power Supply Working Principle for AC to DC converter

According to the above block diagram, the working principle is explained below.

- 1. The first block is the Bridge rectifier circuit. So the input high voltage AC supply(230V) is given to the rectifier and it converted into high voltage DC(230V).
- 2. Then the unfiltered DC is filtered by the filter circuit.

- 3. Then the high voltage DC is converted into very high-frequency square wave AC. Here the high-frequency switch is used to convert DC to AC. The switch is controlled by the feedback and control circuit.
- 4. The high-frequency AC is step down into low voltage (may be 12V, 6V, etc.) by a fly back high-frequency transformer.
- 5. Then again a rectifier circuit is used to convert the low voltage AC to DC.
- 6. A filter circuit is used to filter the DC.

The feedback path and control circuits are used to control the output DC supply. Mainly the Pulse Width Modulation Circuit is used for the control circuit.