CSE 458 Lab Final

Time: 1 Hour

Full Marks: 40

1. **NUMBER** = Your registration number MOD 7 Modify the comparator code given in the classroom such that it has 3 inputs and 1 output. The three inputs represent a decimal value (from 0 to 7) and output is 1 if the value is greater than NUMBER else it is 0. Test all 8 possibility in your testbench. (check example at the bottom if you are confused). Upload the following to classroom a. Verilog code in .v format 5 b. Testbench code in .v format 5 c. Screenshot of the output in .png format 10 2. Consider the following function Y = (A.B) + (C.D)a. Draw Schematic of the function (upload handwriting by scan) 5 b. Draw Euler's path of the function (upload handwriting by scan) 5 5 c. Draw Stick Diagram of the function (upload handwriting by scan) d. Implement the design in Microwind (upload .msk file) 5 3. Consider the following function Y = (A+B).(C+D)a. Draw Schematic of the function (upload handwriting by scan) 5 5 b. Draw Euler's path of the function (upload handwriting by scan) c. Draw Stick Diagram of the function (upload handwriting by scan) 5 d. Implement the design in Microwind (upload .msk file) 5

Example of 1.

My registration number is 0000005

So, Number = 5

So, it will produce the following table:

Х	Υ	Z	OUTPUT
0	0	0	0
0	0	1	0
1	0	1	0
1	1	1	1
1	1	0	1

And so on

You should test all 8 cases.